
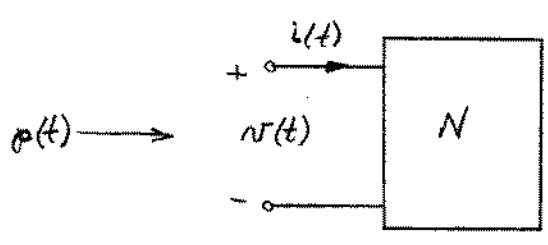


## Basic Principles - Chapter 2

- I. Single Phase Circuits - definitions, real & reactive power, sign conventions, power factor
- II. Conservation of Complex Power - Tellegen's Theorem, two special Two Port Networks  , difference between a bus and a node
- III. Balanced 3 $\phi$  - definition, decoupling,  $\Delta$ - $Y$  Source & Load transformations <sup>of phases</sup>
- IV. Per Phase Analysis - Balanced 3 $\phi$  Theorem
- V. Balanced 3 $\phi$  Power

Other Topics: Phasors, Impedance, Steady State Operation

# I. Complex Power Supplied to a One Port



Let


$$v(t) = V_{max} \cos(\omega t + \theta_V) \quad (2.8)$$

$$i(t) = I_{max} \cos(\omega t + \theta_I) \quad (2.9)$$

Def. Instantaneous Power Delivered to Network N  
(rate at which energy is generated or absorbed by N).

$$p(t) = v(t) i(t)$$
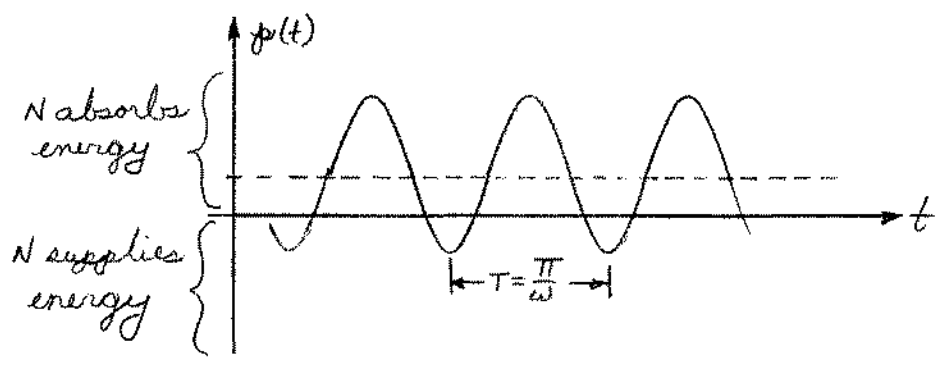
$$= \frac{1}{2} V_{max} I_{max} [\cos(\theta_V - \theta_I) + \cos(2\omega t + \theta_V + \theta_I)] \quad (2.10)$$



$$\omega = 2\pi f = 2\pi 60 \text{ Hz}$$

$$= 377 \text{ rad/sec}$$

$$T = \frac{1}{120} = 8.33 \text{ msec}$$

Def: Power Factor Angle

$$\phi \triangleq \theta_V - \theta_I \quad (2.11)$$

Def: Average Power - accomplished useful work

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_{max} I_{max} \cos \phi \quad (2.12)$$

Decompose  $p(t)$ <sup>1</sup>:

$p(t) = \text{real work} + \text{energy flow in and out of } N,$   
but does no real work

<sup>1</sup> Elgund - Sec 2-3.1 pg 21-27 - use hydraulic analogs

Using trig identities, it can be shown that ( $\theta_I = 0$ )

$$p(t) = \frac{1}{2} V_{\max} I_{\max} [\cos \phi (1 + \cos 2\omega t) - \sin \phi \sin 2\omega t]$$

$$\cos(\alpha + \beta)$$

$$= \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

Def: Real (or Active or Average) Power

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_{\max} I_{\max} \cos \phi$$

Def: Reactive Power

$$Q = \frac{1}{2} V_{\max} I_{\max} \sin \phi$$

$$\therefore p(t) = P(1 + \cos 2\omega t) - Q \sin 2\omega t$$

Sinusoidal Sources }  $\Rightarrow$  phasor notation  
Linear Network

9/16/89  
9/22/02  
9/18/03

### Phasor Notation

$$v(t) = V_{max} \cos(\omega t + \theta_v) \iff \bar{V} = \frac{V_{max}}{\sqrt{2}} e^{j\theta_v} \quad (2.6)$$

similarly

RMS value of sinusoidal

$$i(t) \iff \bar{I} = \frac{I_{max}}{\sqrt{2}} e^{j\theta_i}$$


Then

$$P = \frac{1}{2} V_{max} I_{max} \cos \phi = |\bar{V}| |\bar{I}| \cos \phi$$

$$Q = \frac{1}{2} V_{max} I_{max} \sin \phi = |\bar{V}| |\bar{I}| \sin \phi$$

$\phi$  = power factor angle  
=  $\theta_v - \theta_i$

### Def: Complex Power

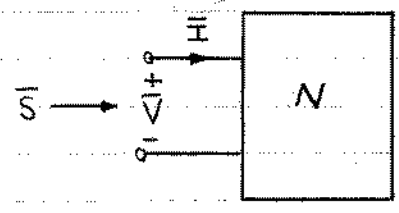

$$\bar{S} \triangleq P + jQ \quad (2.18)$$


$$= |\bar{V}| |\bar{I}| (\cos \phi + j \sin \phi)$$

$$= |\bar{V}| |\bar{I}| e^{j\phi}$$

$$= |\bar{V}| |\bar{I}| e^{j(\theta_v - \theta_i)}$$

$$= (|\bar{V}| e^{j\theta_v}) (|\bar{I}| e^{-j\theta_i})$$

$$= \bar{V} \bar{I}^* \quad (2.17)$$

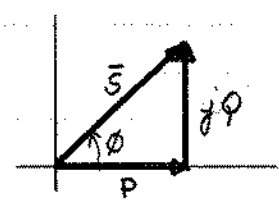

Note: when expressing sinusoidal quantities as phasors, always express the sinusoidal quantity using the "cosine" function

eg.  $v(t) = V_{max} \sin(\omega t + \theta_v) = V_{max} \cos(\omega t + \theta_v - 90^\circ)$

phasor representation of  $v(t)$ :  $\bar{V} = \frac{V_{max}}{\sqrt{2}} e^{j(\theta_v - 90^\circ)}$

	> 0	< 0
P (Watts, W, kW, MW)	N absorbs real power (i.e. load)	N generates real power (i.e. generator)
Q (Volt- ampere reactive: VAR, kVAR, MVAR)	N absorbs reactive power (i.e. inductive load) <ul style="list-style-type: none"> <li>• I lags V</li> <li>• lagging PF load</li> <li>• <math>\phi &gt; 0</math></li> </ul>	N supplies reactive power (i.e. capacitive load) <ul style="list-style-type: none"> <li>• I leads V</li> <li>• leading PF load</li> <li>• <math>\phi &lt; 0</math></li> </ul>

Def: Power Factor  $PF \triangleq \cos \phi$

## II. Conservation of Complex Power

### Theorem of Conservation of Complex Power

$$\sum \text{complex power supplied by ind. sources} = \sum \text{complex power received by all other branches} \iff \sum_{k=1}^b \bar{S}_k = 0$$

Proof: Use Tellegen's Theorem

↑  
one port representation

Tellegen's Theorem (without proof):

If a set of voltages  $v_1'(t), v_2'(t), \dots, v_b'(t)$  satisfy KVL around all loops in a network; and if a set of currents  $i_1''(t), i_2''(t), \dots, i_b''(t)$  satisfy KCL at all nodes in a network, then

$$\sum_{\text{all branches}} v_k'(t) i_k''(t) = 0$$

where  $v_k'(t)$  and  $i_k''(t)$  refer to the voltage across and current thru the  $k$ -th branch

Note:  $v_k'(t)$  and  $i_k''(t)$  do not need to be related via ohm's law!

If we do let  $v_k'$  and  $i_k''$  be related by ohm's law, then  $v_k' i_k'' = p_k$  and we have

$$\sum_{\text{all branches}} p_k(t) = 0$$

"Summation of instantaneous power  $p(t)$  for  $b$  branches in the network must be zero"

Other Uses of Tellegen's Theorem

1) Network Sensitivity Calculations - Adjoint Sensitivity Method


Tellegen's Theorem can be extended to phasors (sinusoidal s.s.)

KVL is valid for  $\bar{V}$  as well as  $v(t)$

KCL " " "  $\bar{I} \bar{I}^*$  " "  $i(t)$

Then
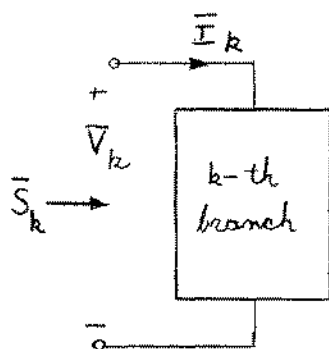
$$\sum_{k=1}^b v_k(t) i_k(t) = 0 \iff \sum_{k=1}^b \bar{V}_k \bar{I}_k^* = 0$$




$$\sum_{k=1}^b \bar{S}_k = 0$$

Note:


Complex Power is NOT summed into a node.

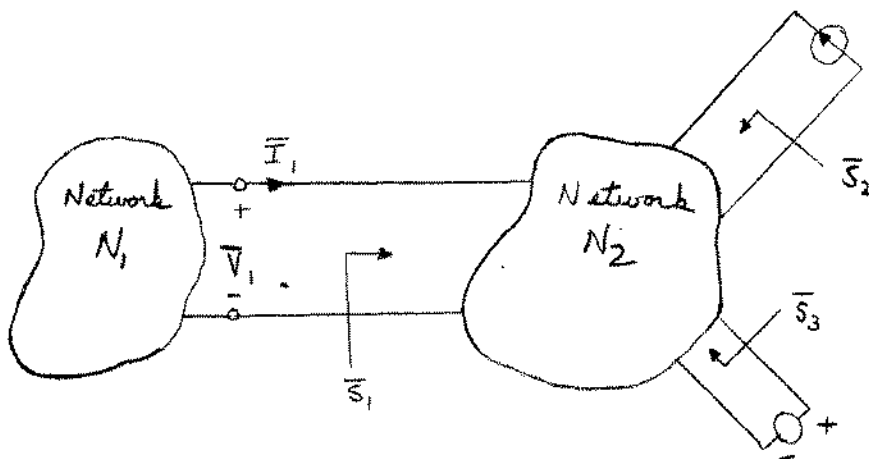Bus - a common connecting point for two or more 3 $\phi$  elements  
(K uses page 36)



$$\begin{aligned} & \bar{S}_1 + \bar{S}_2 + \bar{S}_3 \\ &= \sum \bar{S}_i \\ & \quad i = \text{elements} \\ & \quad \text{in } N_2 \end{aligned}$$

## Example 2.4

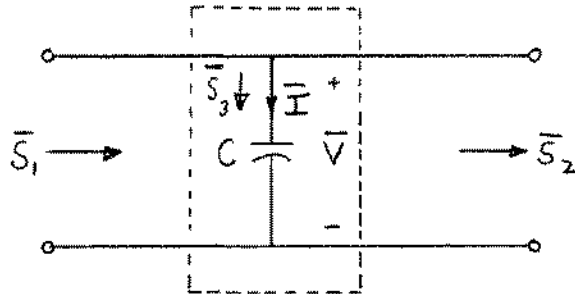

Find  $\bar{S}_2$  in terms of  $\bar{S}_1$ ,  $C$ ,  $\bar{V}$

Sol<sup>n</sup>

• Theorem of Conservation of Complex Power  $\bar{S}_2 = \bar{S}_1 - \bar{S}_3$

•  $\bar{S}_3 = \bar{V} \bar{I}^*$

$$= \bar{V} (j\omega C \bar{V})^* = -j\omega C |\bar{V}|^2$$

•  $\bar{S}_2 = \bar{S}_1 - \bar{S}_3$

$$= \bar{S}_1 + j\omega C |\bar{V}|^2 = P_1 + jQ_1 + j\omega C |\bar{V}|^2$$

$$= P_2 + jQ_2$$

$$P_2 = P_1$$

$$Q_2 = Q_1 + \omega C |\bar{V}|^2$$


• Note: ①  $Q_2 > Q_1$ , capacitor acts as a source of reactive power

② no gain or loss of real power

③  $Q_2 \propto |\bar{V}|^2$

②  
9/16/89  
9/22/02

Example 2.5

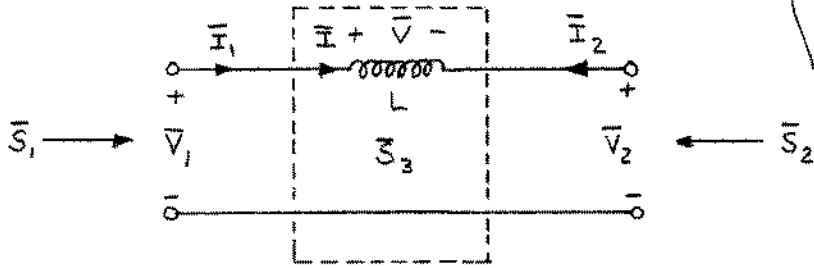

It can be shown using the conservation of complex power that:

$$\bar{S}_2 = -\bar{S}_1^* \quad \text{when} \quad |\bar{V}_2| = |\bar{V}_1|$$

Let  $\bar{S}_1 = P_1 + jQ_1$   
then  $\bar{S}_2 = -P_1 + jQ_1$

- ① no loss in real power
- ② Port 1 & Port 2 each supply exactly  $\frac{1}{2}$  of total reactive power absorbed by L

Sol<sup>n</sup>

• Theorem of Conservation of Complex Power:  $\bar{S}_1 + \bar{S}_2 = \bar{S}_3$

•  $\bar{S}_3 = \bar{V} \bar{I}^*$   
 $= (j\omega L \bar{I}) \bar{I}^*$   
 $= j\omega L |\bar{I}|^2$

•  $\bar{S}_1 = \bar{V}_1 \bar{I}_1^* = \bar{V}_1 \bar{I}^*$

$\bar{S}_2 = \bar{V}_2 \bar{I}_2^* = -\bar{V}_2 \bar{I}^*$

• If  $|\bar{V}_1| = |\bar{V}_2|$ , then  $|\bar{S}_1| = |\bar{S}_2| \Rightarrow |P_1| = |P_2|$   
 $|Q_1| = |Q_2|$

• Since  $\bar{S}_1 + \bar{S}_2 = \bar{S}_3 = 0 + j\omega L |\bar{I}|^2$

$P_1 = -P_2$

$Q_1 + Q_2 = \omega L |\bar{I}|^2$



$\therefore Q_1 = Q_2 = \frac{1}{2} \omega L |\bar{I}|^2$

•  $\left. \begin{aligned} \bar{S}_1 &= P_1 + j \frac{1}{2} \omega L |\bar{I}|^2 \\ \bar{S}_2 &= -P_1 + j \frac{1}{2} \omega L |\bar{I}|^2 \end{aligned} \right\} \Rightarrow \bar{S}_2 = -\bar{S}_1^*$

### III. Balanced 3 $\phi$

Definition

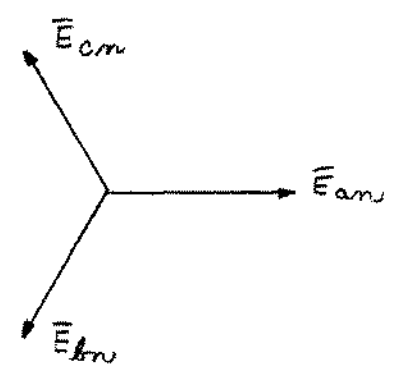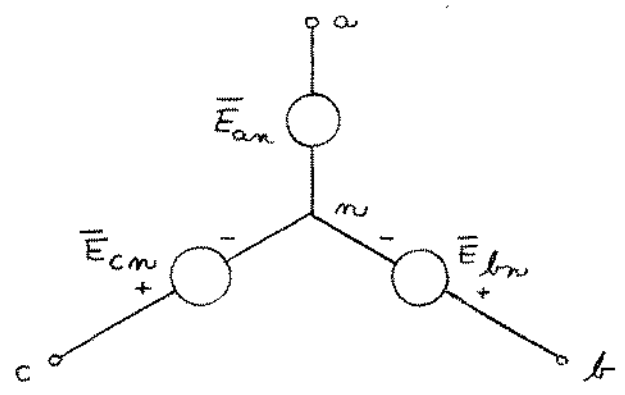- 1) Sources: balanced 3 $\phi$  w/ same phase sequence
- 2) Network: possesses 3 $\phi$  symmetry



$$\bar{E}_{an} = 1 \angle 0^\circ$$

$$\bar{E}_{an} + \bar{E}_{bn} + \bar{E}_{cn} = 0$$


$$\bar{E}_{bn} = 1 \angle -120^\circ$$

$$\bar{E}_{cn} = 1 \angle -240^\circ$$

$$e_{an}^{(t)} = \sqrt{2} |\bar{E}_{an}| \cos(\omega t + 0^\circ)$$

$$e_{bn}^{(t)} = \sqrt{2} |\bar{E}_{bn}| \cos(\omega t - 120^\circ)$$

$$e_{cn}^{(t)} = \sqrt{2} |\bar{E}_{cn}| \cos(\omega t - 240^\circ)$$

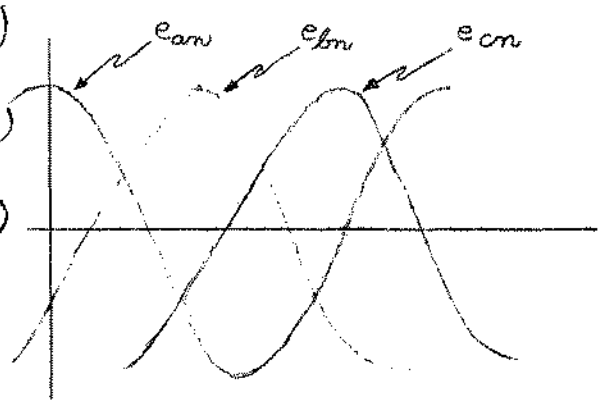

"a" reaches "+" max 1<sup>st</sup>  
 "b" " " " 2<sup>nd</sup>  
 "c" " " " 3<sup>rd</sup>


$$\bar{E}_{ab} = \bar{E}_{an} - \bar{E}_{bn} = \sqrt{3} |\bar{E}_{an}| \angle 30^\circ$$

$$\bar{E}_{bc} = \bar{E}_{bn} - \bar{E}_{cn} = \sqrt{3} |\bar{E}_{an}| \angle -90^\circ$$

$$\bar{E}_{ca} = \bar{E}_{cn} - \bar{E}_{an} = \sqrt{3} |\bar{E}_{an}| \angle -210^\circ$$

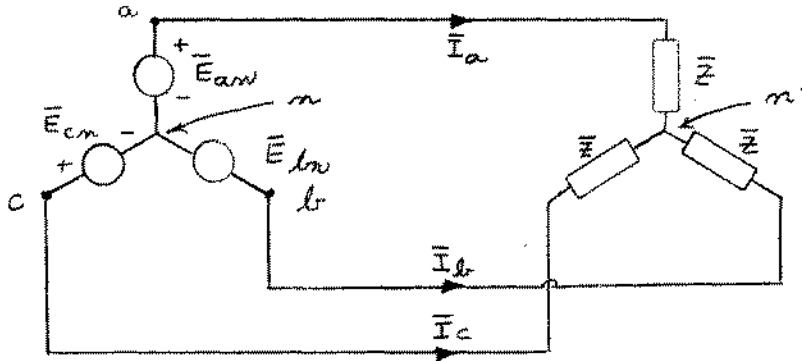Example 2.9 - Illustrates the concept of "Decoupling of Phases" in Balanced 3φ Systems

$\bar{E}_{an}, \bar{E}_{bn}, \bar{E}_{cn}$  are balanced



$$\bar{Y} = 1/\bar{Z}$$

$$\begin{aligned} \bar{I}_a &= \bar{Y} (\bar{E}_{an} + \bar{V}_{mn'}) \\ \bar{I}_b &= \bar{Y} (\bar{E}_{bn} + \bar{V}_{mn'}) \\ \bar{I}_c &= \bar{Y} (\bar{E}_{cn} + \bar{V}_{mn'}) \end{aligned}$$


By KCL:  $\bar{I}_a + \bar{I}_b + \bar{I}_c = 0$

$$\therefore \bar{Y} (\underbrace{\bar{E}_{an} + \bar{E}_{bn} + \bar{E}_{cn}}_{= 0, \text{ since they are balanced}} + 3\bar{V}_{mn'}) = 0$$

$\therefore \bar{V}_{mn'} = 0$   
and




$$\left. \begin{aligned} \bar{I}_a &= \bar{Y} \bar{E}_{an} \\ \bar{I}_b &= \bar{Y} \bar{E}_{bn} \\ \bar{I}_c &= \bar{Y} \bar{E}_{cn} \end{aligned} \right\} \text{phases are "decoupled"}$$

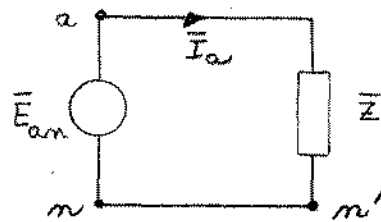Solve 1φ circuit, instead of all 3φ circuits



This result can be generalized to more complicated balanced 3φ systems

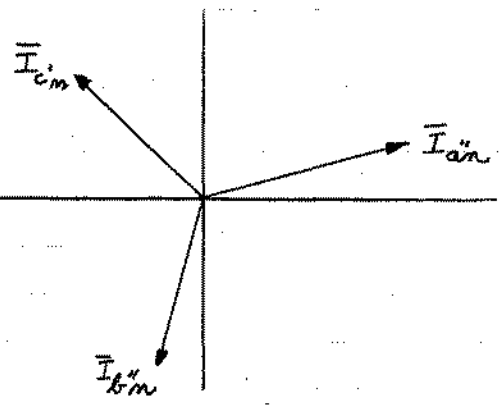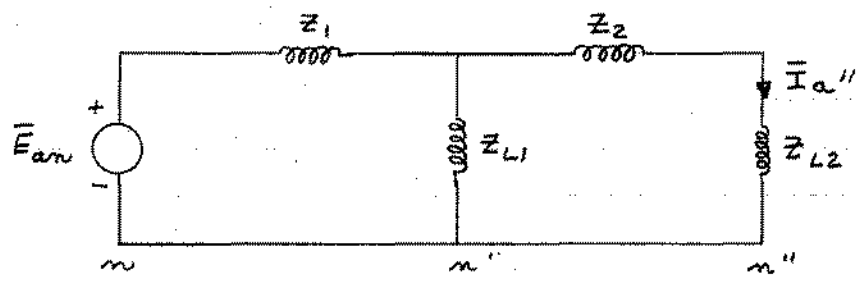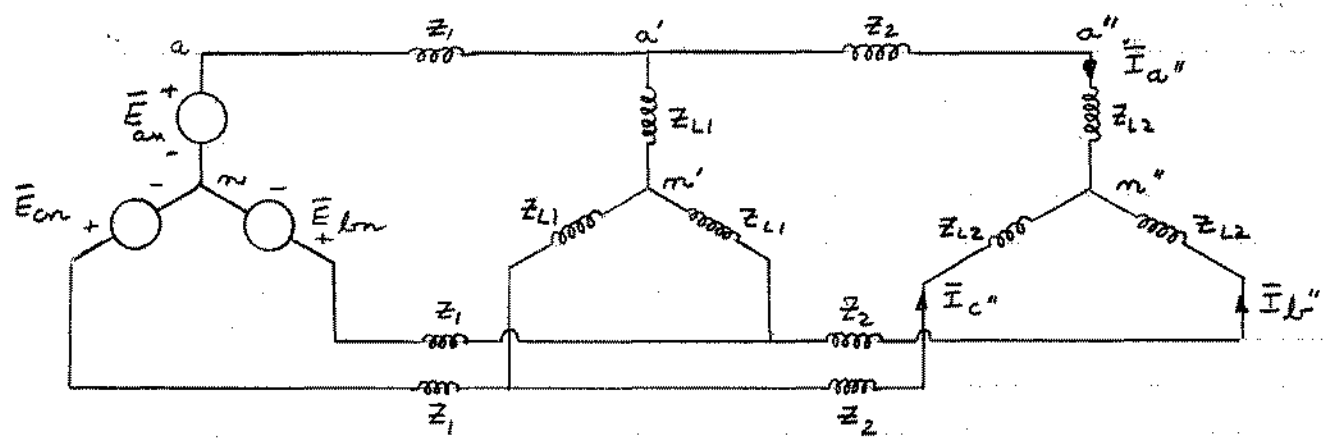
Note: Sources and loads must be Y connected for decoupling of phases to occur



In a balanced 3 $\phi$  system, it is only necessary to analyze one phase. The other 2 $\phi$  are 120° & 240° out of phase.


## $\Delta - Y$ Transformation

### Balanced Load

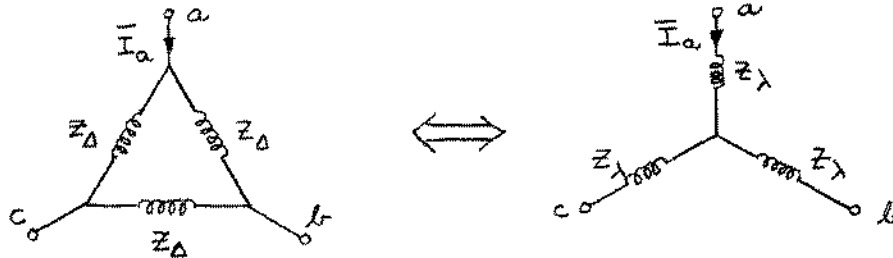

$$Z_Y = Z_D / 3$$

### Balanced Sources

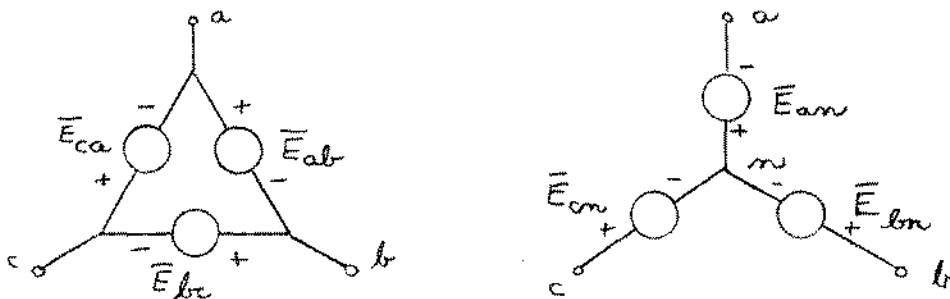

$$\text{Positive Sequence} \begin{cases} \bar{E}_{ab} = \sqrt{3} e^{j\pi/6} \bar{E}_{an} & (2.30) \\ \bar{E}_{an} = \frac{1}{\sqrt{3}} e^{-j\pi/6} \bar{E}_{ab} & (2.31) \end{cases}$$

We'll consider "Negative Sequence" quantities when we cover Unbalanced System Operation.

#### IV. Per Phase Analysis (addresses voltage & current only, not power)

##### Balanced 3 $\phi$ Theorem

If

1. system is balanced 3 $\phi$
2. all loads and sources are Y-connected
3. no mutual inductance between phases

Then

1. all neutrals are at the same potential
2. all phases are completely decoupled
3. all corresponding network variables occur in balanced sets of the same sequence as the source

##### Per Phase Analysis

Given a balanced 3 $\phi$  circuit with no mutual inductance between phases

1. convert all  $\Delta$  sources & loads into equiv Y connections
2. solve for the desired "phase a" variable (voltage or current) using "phase a" circuit with all neutrals connected together
3. phase b & c variables can be readily calculated
  - subtract  $120^\circ$  from "phase a" to obtain "phase b"
  - " "  $240^\circ$  " " " " " " " c
4. if necessary, go back to the original circuit to find line-line variables or variables internal to  $\Delta$  connections

## V. Balanced 3 $\phi$ Power

### A. Complex Power

$$\begin{aligned}
 \bar{S}_{3\phi} &= \bar{V}_{an} \bar{I}_a^* + \bar{V}_{bn} \bar{I}_b^* + \bar{V}_{cn} \bar{I}_c^* \\
 &= \bar{V}_{an} \bar{I}_a^* + \bar{V}_{an} e^{-j120^\circ} \bar{I}_a^* e^{j120^\circ} + \bar{V}_{an} e^{-j240^\circ} \bar{I}_a^* e^{j240^\circ} \\
 &= \bar{V}_{an} \bar{I}_a^* (1 + 1 + 1) \\
 &= 3 \bar{V}_{an} \bar{I}_a^* \tag{2.34}
 \end{aligned}$$

### B. Real Power

$$p_{3\phi}(t) = v_a(t) i_a(t) + v_b(t) i_b(t) + v_c(t) i_c(t)$$

It can be shown (using trig identities) that

$$\begin{aligned}
 p_{3\phi}(t) &= 3 |\bar{V}| |\bar{I}| \cos \phi \\
 &= 3P \tag{2.37}
 \end{aligned}$$

Note that instantaneous power supplied is constant.