

Rules

Single Phase

1. Base values must satisfy ohm's law & power equation

$$a. \quad V_B = Z_B I_B$$

$$\frac{\bar{V}}{V_B} = \frac{\bar{Z}}{Z_B} \frac{\bar{I}}{I_B} \Rightarrow \bar{V}_{pu} = \bar{Z}_{pu} \bar{I}_{pu}$$

$$b. \quad S_B = V_B I_B$$

$$\frac{\bar{S}}{S_B} = \frac{\bar{V} \bar{I}^*}{V_B I_B} \Rightarrow \bar{S}_{pu} = \bar{V}_{pu} \bar{I}_{pu}^*$$

$$\frac{\bar{S}}{S_B} = \frac{P}{S_B} + j \frac{Q}{S_B} \quad \bar{S}_{pu} = P_{pu} + j Q_{pu}$$

2. There are 2 independent base values (\neq)

$$\left. \begin{array}{l} V_B = Z_B I_B \\ S_B = V_B I_B \end{array} \right\} \text{2 equations in 4 unknowns}$$

Normally select V_B & S_B , and then solve for I_B & Z_B

S_B is held fixed for entire system.

V_B changes (due to transformers)

$$Z_B = \frac{V_B^2}{S_B}$$

$$I_B = \frac{S_B}{V_B}$$

8/24/84


Rules (cont'd)
5. Transformers

general approach: choose different base voltage values on each side of a transformer

rule: Ratio of Voltage Bases = Connection Induced Voltage Magnitude Ratio in the per phase equivalent ckt

a) Y-Y

see pg 132-133 in Bergen

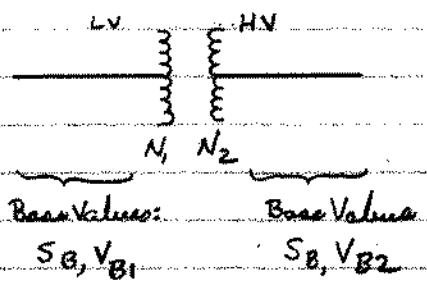


let X_l = leakage reactance
 X_m = magnetizing reactance

applying rule: $\frac{V_{B2}}{V_{B1}} = \frac{N_2}{N_1} = n$

then $Z_{B1} = \frac{V_{B1}^2}{S_B}$ and $Z_{B2} = \frac{V_{B2}^2}{S_B}$


Per Phase Diagram

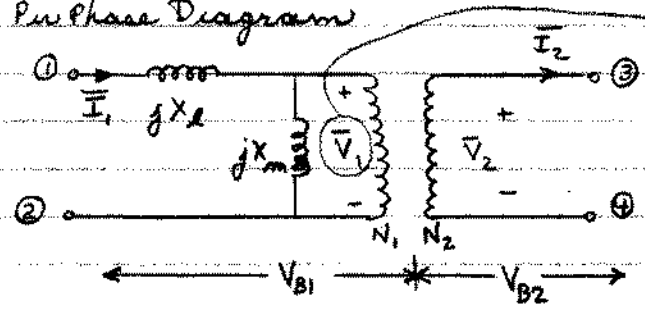

since $\bar{V}_{1,pu} = \frac{\bar{V}_1}{V_{B1}}$

$\bar{V}_{2,pu} = \frac{\bar{V}_2}{V_{B2}} = \frac{n\bar{V}_1}{nV_{B1}} = \bar{V}_{1,pu}$


∴ ideal transformer can be eliminated

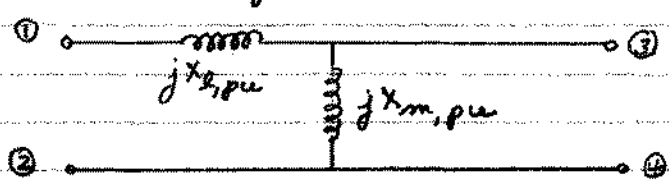

$jX_{l,pu} = \frac{jX_l}{Z_{B1}}$ $jX_{m,pu} = \frac{jX_m}{Z_{B1}}$

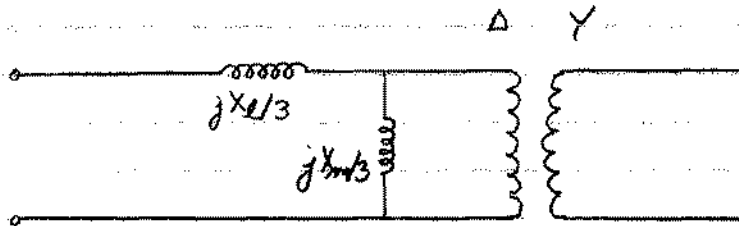b) Δ -Y
 ↑ ↑
 LV HV

Simplified Per Phase Diagram (all phase shifts left out)




Base Values
 S_B, V_{B1}

Base Values
 S_B, V_{B2}

applying rule

ratio of voltage bases $\Rightarrow \frac{V_{B2}}{V_{B1}} = \sqrt{3} n \leftarrow$ connection induced voltage magnitude ratio in per phase equiv. ckt

c) Y- Δ
 ↑ ↑
 LV HV

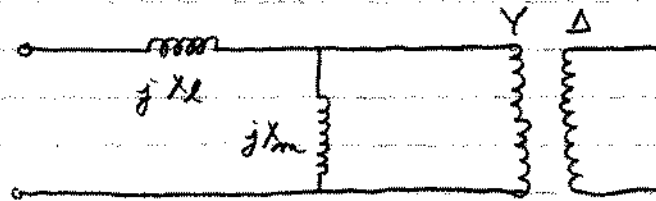

S_B, V_{B1}

S_B, V_{B2}

$$\frac{V_{B2}}{V_{B1}} = |K_3| = \frac{n}{\sqrt{3}}$$

d) Δ - Δ

$$\frac{V_{B2}}{V_{B1}} = \frac{N_2}{N_1}$$

6. Changing Base

Let $Z_{pu}^{old} = \text{pu impedance based on nameplate rating} = \frac{Z^{actual}}{Z_B^{old}}$

where

$$Z_B^{old} = \frac{(V_{nameplate})^2}{S_{nameplate}} \quad (V_B^{old}, S_B^{old}) \text{ or } (V_B, S_B)$$

$Z^{actual} = \text{impedance before pu normalization}$

Since all equipment in the system will not have the same nameplate ratings for V & S , we will arbitrarily select the nameplate ratings from one piece of equipment as the reference, and then adjust the pu impedances of the remaining equipment as follows:

$$Z_{pu}^{new} = \frac{Z^{actual}}{Z_B^{new}}$$

where

$Z_B^{new} = \text{new base impedance}$

then

$$\begin{aligned}
 Z_{pu}^{new} &= Z_{pu}^{old} \left[\frac{Z_B^{old}}{Z_B^{new}} \right] \\
 &= Z_{pu}^{old} \left[\frac{V_B^{old}}{V_B^{new}} \right]^2 \frac{S_B^{new}}{S_B^{old}}
 \end{aligned}$$

(5.33)

nameplate value

Per Unit Analysis of Normal Systems

- (a) Pick a common three-phase MVA base for the entire system
- (b) In one part of the system, arbitrarily pick a line-to-line kV base
- (c) Relate the line-to-line kV bases across transformers according to the ratio of nameplate line-to-line kV ratings of 3 ϕ transformers
- (d) Find the impedance bases in different sections according to the formula

$$Z_B = \frac{(V_B^{ll})^2}{S_B^{3\phi}}$$

- (e) Adjust all equipment nameplate per-unit impedances according to the base values.
- (f) Draw the impedance diagram for the entire system, and solve for desired per-unit quantities
- (g) Convert back to actual quantities if desired


10/13/03
8/24/04

Example 5.11

Given a 1 ϕ transformer

Nameplate Data : 1000 KVA, 13.2-66 kV, $X_l = 0.1 \text{ pu}$, $X_m = 100 \text{ pu}$

a) On 13.2 kV side

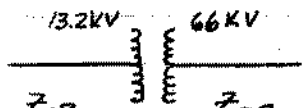

$$Z_{1B} = \frac{V_{1B}^2}{S_B} = \frac{(13.2 \times 10^3)^2}{1000 \times 10^3} = 174 \Omega \Rightarrow X_l = X_l^{\text{pu}} \cdot 174 = 0.1 \times 174 = 17.4 \Omega$$

$$X_m = X_m^{\text{pu}} \cdot 174 = 100 \times 174 = 17,400 \Omega$$

b) On 66 kV side

$$Z_{2B} = \frac{V_{2B}^2}{S_B} = \frac{(66 \times 10^3)^2}{1000 \times 10^3} = 4356 \Omega \Rightarrow X_l = 0.1 \times 4356 = 435.6 \Omega$$

$$X_m = 100 \times 4356 = 435,600 \Omega$$

c) 3 ϕ Connections

1. Y- Δ or Y-Y

$$S_B^{3\phi} = 3 \times 1000 \text{ kVA} = 3000 \text{ kVA}$$

$$V_B^{\text{ll}} = \sqrt{3} \cdot 13.2 \text{ kV}$$

$$Z_B = \frac{(V_B^{\text{ll}})^2}{S_B^{3\phi}} = \frac{(\sqrt{3} \cdot 13.2 \text{ kV})^2}{3000 \times 10^3} = 174 \Omega$$

$$\therefore X_l^{\text{pu}} = \frac{17.4}{174} = 0.1 \text{ pu}$$

$$X_m^{\text{pu}} = \frac{17,400}{174} = 100 \text{ pu}$$

2. Δ -Y or Δ - Δ


$$S_B^{3\phi} = 3000 \text{ kVA}$$

$$V_B^{\text{ll}} = 13.2 \text{ kV}$$

$$Z_{1B} = \frac{(13.2 \text{ kV})^2}{3000 \times 10^3} = 58.1 \Omega$$

$$\therefore X_l^{\text{pu}} = \frac{17.4/3}{58.1} = 0.1 \text{ pu}$$
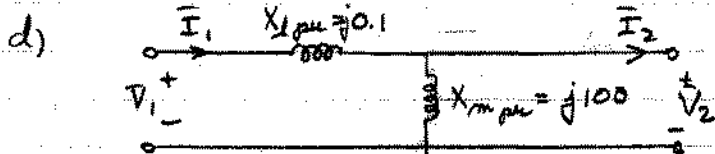
$$X_m^{\text{pu}} = \frac{17,400/3}{58.1} = 100 \text{ pu}$$




Important:

As long as we use the nameplate V & S as the basis, then the pu impedances in the "per phase" diagram are the same as the 1 ϕ nameplate values.

8/24/04

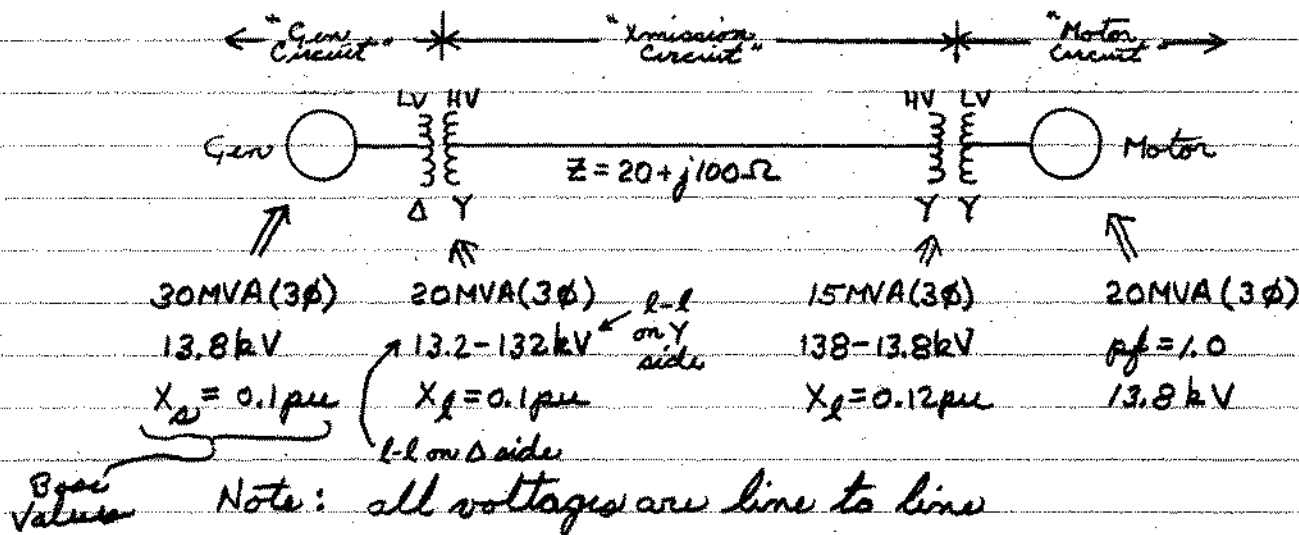Ex: Draw an impedance diagram for the following system




Solution


	Gen Circuit	Transmission Circuit	Motor Circuit
$S_B^{3\phi}$ (MVA)	30	30	30
V_B^L (kV)	13.8	$13.8 \times \frac{132}{13.2} = 138$	$138 \times \frac{13.8}{138} = 13.8$
$Z_B (\Omega)$	Not Needed	$\frac{(V_B^L)^2}{S_B^{3\phi}} = 634.8 \Omega$	Not Needed
I_B (A)	$\frac{S_B^{3\phi}}{\sqrt{3} V_B^L} = 1255.1$	$\frac{S_B^{3\phi}}{\sqrt{3} V_B^L} = 125.5$	$\frac{S_B^{3\phi}}{\sqrt{3} V_B^L} = 1255.1$

$$Z_{pu}^{new} = Z_{pu}^{old} \left(\frac{V_B^{old}}{V_B^{new}} \right)^2 \frac{S_B^{new}}{S_B^{old}} = 0.1 \left(\frac{13.2}{13.8} \right)^2 \left(\frac{30}{20} \right) =$$
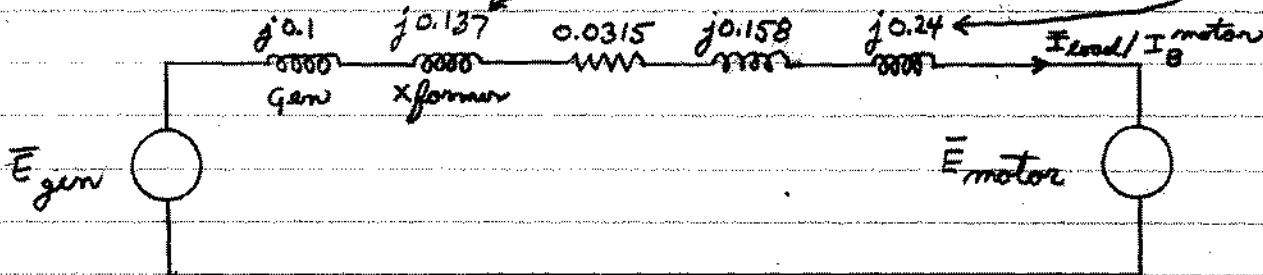
$$Z_{pu}^{new} = 0.12 \left(\frac{13.8}{13.8} \right)^2 \left(\frac{30}{15} \right) =$$




Example: Draw the impedance diagram for the following system.
 Choose a base of 50MVA and 13.8kV in the circuit of generator 1.

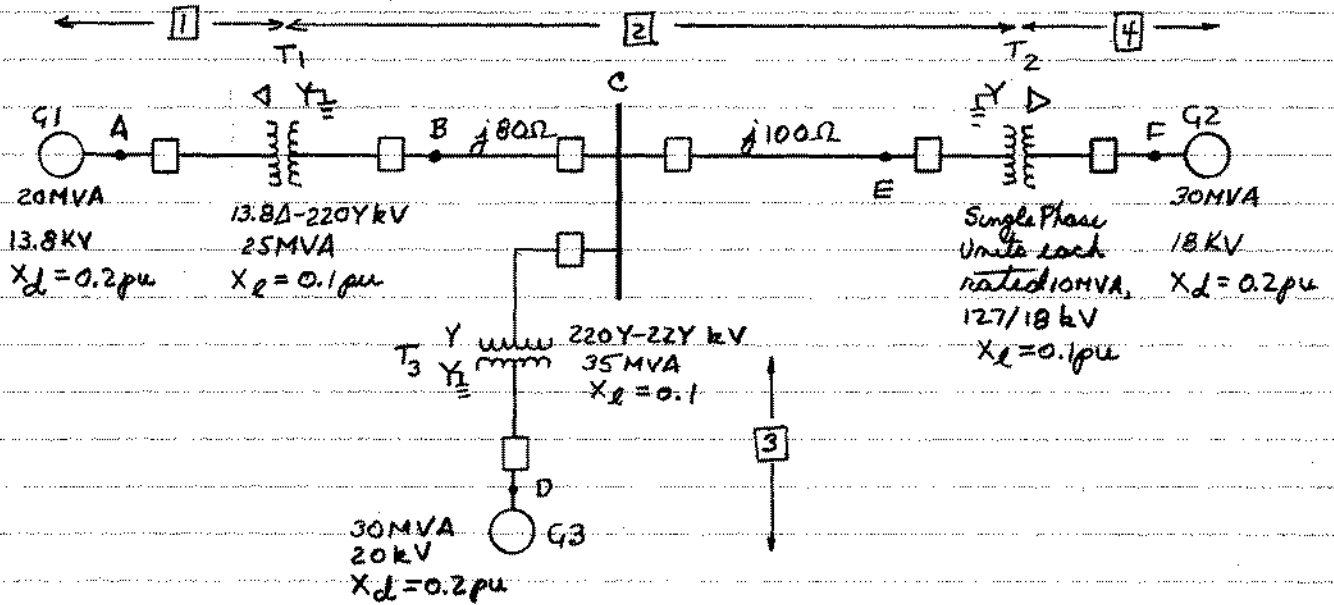

Side I: $S_B^{3\phi} = 50 \text{ MVA}$ $V_B^{ll} = 13.8 \text{ kV}$

Generator G1:

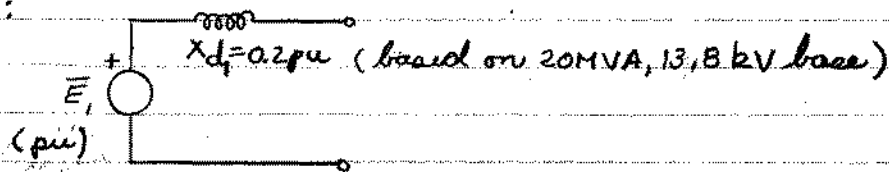

$$X_{d1}^{new} = X_{d1} \left(\frac{V_B^{ll(alt)}}{V_B^{ll(new)}} \right)^2 \left(\frac{S_B^{new}}{S_B^{old}} \right) = 0.2 \left(\frac{13.8}{13.8} \right)^2 \left(\frac{50}{20} \right) = 0.5 \text{ pu}$$

Transformer T1:

$$X_{l1} \text{ on } \Delta \text{ side} = 0.1 \text{ pu} \quad (\text{based on } 25 \text{ MVA, } 13.8 \text{ kV base})$$

$$X_{l1}^{new} = 0.1 \left(\frac{13.8}{13.8} \right)^2 \left(\frac{50}{25} \right) = 0.2 \text{ pu}$$

Side [2] $S_B^{3\phi} = 50 \text{ MVA}$ $V_B^{ll} = 220 \text{ kV}$

11/4/02
10/20/03

$$Z_B = \frac{(V_B^{ll})^2}{S_B^{3\phi}} = \frac{220^2}{50} = 968 \Omega$$

Transmission Line BC: $X_{BC} = \frac{80}{968} = 0.083 \text{ pu}$

Transmission Line CE: $X_{CE} = \frac{100}{968} = 0.103 \text{ pu}$

Transformer T1: $X_{L1}^{new} = 0.1 \left(\frac{220}{220}\right)^2 \left(\frac{50}{25}\right) = 0.2 \text{ pu}$ (same as for side [1])

Transformer T2: $X_{L2}^{new} = 0.1 \left(\frac{\sqrt{3} \cdot 127}{220}\right)^2 \left(\frac{50}{3.10}\right) = 0.166 \text{ pu}$

Transformer T3: $X_{L3}^{new} = 0.1 \left(\frac{220}{220}\right)^2 \left(\frac{50}{35}\right) = 0.143 \text{ pu}$

Side [3] $S_B^{3\phi} = 50 \text{ MVA}$ $V_B^{ll} = 22 \text{ kV}$


Generator G3: $X_{d3}^{new} = 0.2 \left(\frac{20}{22}\right)^2 \left(\frac{50}{30}\right) = 0.275 \text{ pu}$

Transformer T3: $X_{L3}^{new} = 0.1 \left(\frac{22}{22}\right)^2 \left(\frac{50}{35}\right) = 0.143 \text{ pu}$ (same as for side [2])

Side [4] $S_B^{3\phi} = 50 \text{ MVA}$ $V_B^{ll} = 220 \times \frac{18}{127\sqrt{3}} = 18 \text{ kV}$


Generator G2: $X_{d2}^{new} = 0.2 \left(\frac{18}{18}\right)^2 \left(\frac{50}{30}\right) = 0.333 \text{ pu}$

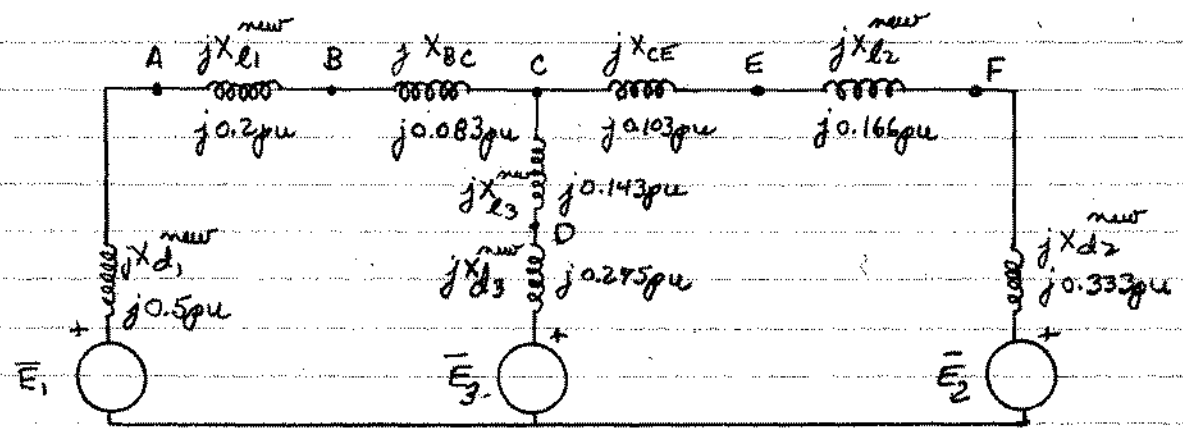Transformer T2: $X_{L2}^{new} = 0.1 \left(\frac{18}{18}\right)^2 \left(\frac{50}{3.10}\right) = 0.166 \text{ pu}$ (same as for side [2])



Transmission Lines and Transformers

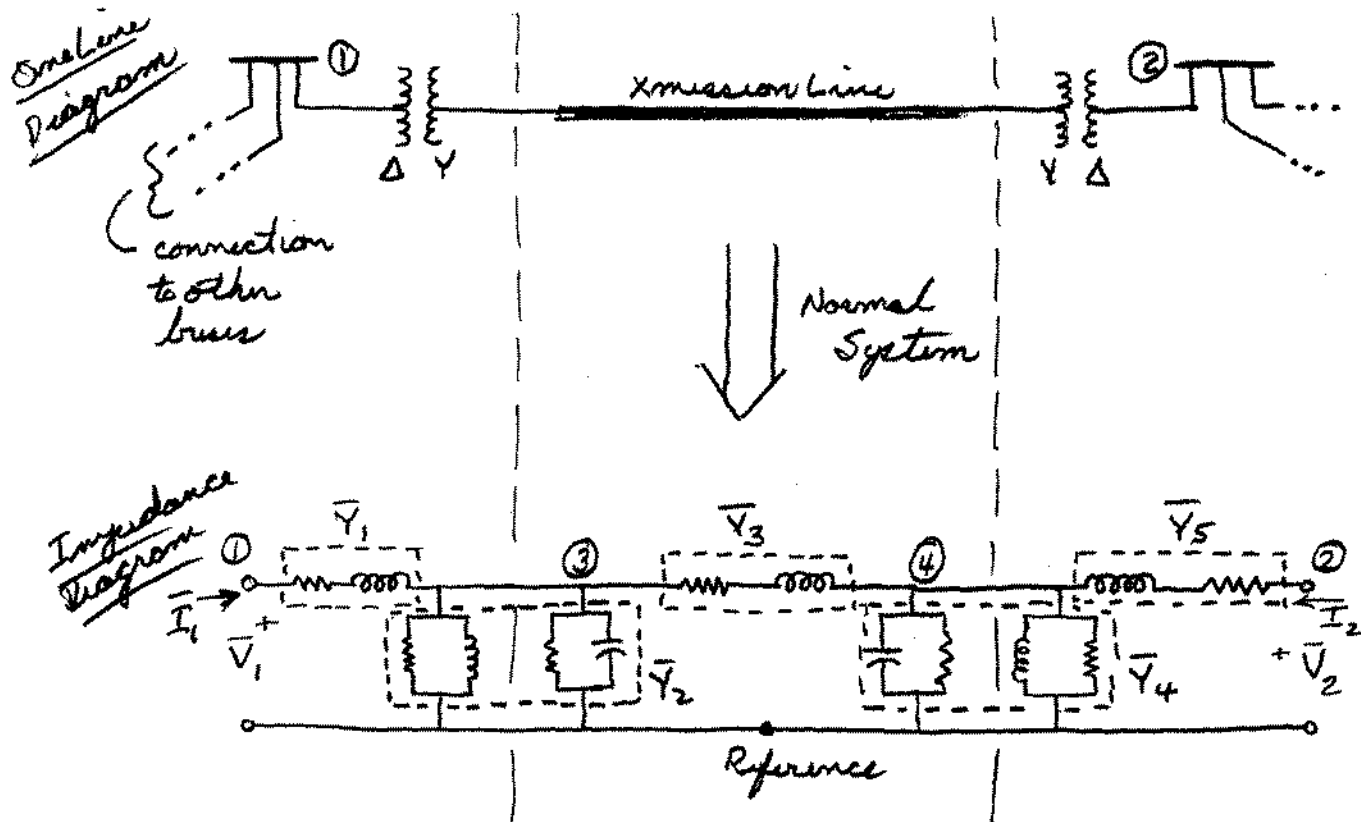
Let us consider a typical transmission line / transformer connection between two buses in a power system



Number of nodes in the Impedance Diagram above? $4 + 1$
↑
Reference

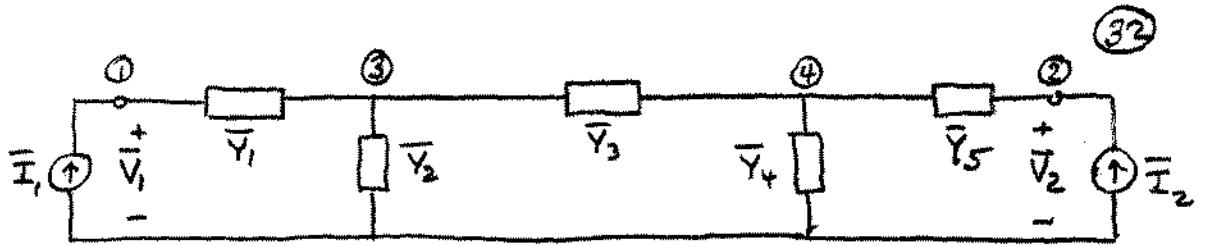In power system calculations, the currents \bar{I}_1 & \bar{I}_2 are often known, and the voltages \bar{V}_1 & \bar{V}_2 need to be determined. Let us add current sources at the ends of the Impedance Diagram





The node equations:

<u>node</u>	<u>equation</u>	
①	$\bar{I}_1 = \bar{Y}_1 (\bar{V}_1 - \bar{V}_3)$	} Linear $E_{\bar{I}}^m$
②	$\bar{I}_2 = \bar{Y}_5 (\bar{V}_2 - \bar{V}_4)$	
③	$0 = \bar{Y}_3 (\bar{V}_3 - \bar{V}_4) + \bar{Y}_2 (\bar{V}_3 - 0) + \bar{Y}_1 (\bar{V}_3 - \bar{V}_1)$	
④	$0 = \bar{Y}_3 (\bar{V}_4 - \bar{V}_3) + \bar{Y}_4 (\bar{V}_4 - 0) + \bar{Y}_5 (\bar{V}_4 - \bar{V}_2)$	

$\underbrace{\hspace{10em}}$
 current sources
 (connected to reference)

Put in matrix form:

$$\begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} \bar{Y}_1 & 0 & -\bar{Y}_1 & 0 \\ 0 & \bar{Y}_5 & 0 & -\bar{Y}_5 \\ -\bar{Y}_1 & 0 & \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 & -\bar{Y}_3 \\ 0 & -\bar{Y}_5 & -\bar{Y}_3 & \bar{Y}_3 + \bar{Y}_4 + \bar{Y}_5 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \\ \bar{V}_3 \\ \bar{V}_4 \end{bmatrix}$$

$$\begin{bmatrix} \underline{\bar{I}} \\ \underline{0} \end{bmatrix} = \underbrace{\begin{bmatrix} A_{11} & A_{12} \\ A_{21} & A_{22} \end{bmatrix}}_{=\bar{Y}} \begin{bmatrix} \underline{V} \\ \underline{V}' \end{bmatrix} \quad (*)$$

known unknown

A number of methods to solve Eq (*) for $\bar{V}_1, \bar{V}_2, \bar{V}_3, \bar{V}_4$.
One method is to invert $[Y]$.

$$\begin{bmatrix} \underline{V} \\ \underline{V}' \end{bmatrix} = [Z] \begin{bmatrix} \underline{I} \\ \underline{0} \end{bmatrix} \quad \text{where } [Z] = [Y]^{-1}$$

Alternate Method

- In many power system studies, one is usually interested in determining \bar{V}_1 and \bar{V}_2 . The other voltages (\bar{V}_3 and \bar{V}_4) can be calculated once \bar{V}_1 & \bar{V}_2 are known.
- Extract equations for nodes ③ and ④ from Eq (*)

$$\begin{bmatrix} \underline{0} \\ \underline{0} \end{bmatrix} = \underbrace{\begin{bmatrix} -\bar{Y}_1 & 0 \\ 0 & -\bar{Y}_5 \end{bmatrix}}_{[A_{21}]} \underbrace{\begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix}}_{\underline{V}} + \underbrace{\begin{bmatrix} \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 & -\bar{Y}_3 \\ -\bar{Y}_3 & \bar{Y}_3 + \bar{Y}_4 + \bar{Y}_5 \end{bmatrix}}_{[A_{22}]} \underbrace{\begin{bmatrix} \bar{V}_3 \\ \bar{V}_4 \end{bmatrix}}_{\underline{V}'}$$

- Solve for \underline{V}'

$$\underline{V}' = -[A_{22}]^{-1} [A_{21}] \underline{V} \quad (**)$$


- From Eq (*), write the node equations corresponding to nodes ① and ②

$$\underline{I} = [A_{11}] \underline{V} + [A_{12}] \underline{V}' \quad (***)$$

- Eliminate \underline{V}' from (***) by substituting (**) for \underline{V}'

$$\begin{aligned} \underline{I} &= [A_{11}] \underline{V} + [A_{12}] (-[A_{22}]^{-1} [A_{21}] \underline{V}) \\ &= ([A_{11}] - [A_{12}] [A_{22}]^{-1} [A_{21}]) \underline{V} = [Y'] \underline{V} \end{aligned}$$

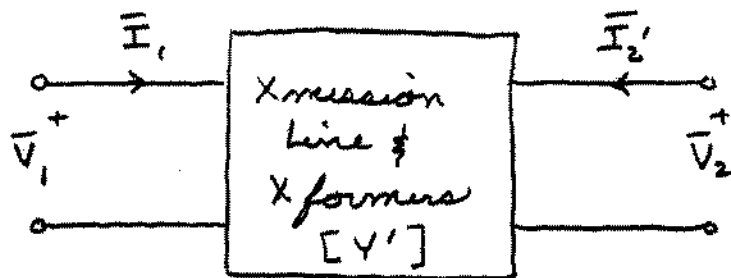Equivalent two-port representation of transmission line and transformer



We can solve the equation on the bottom of the previous page for \bar{V}_1 and \bar{V}_2 . Once these are found, then \bar{V}_3 and \bar{V}_4 can be determined.

Example

Let $\bar{z}_1 = \bar{z}_3 = \bar{z}_5 = j0.1 \therefore \bar{Y}_1 = \bar{Y}_3 = \bar{Y}_5 = -j10$
 $\bar{Y}_2 = \bar{Y}_4 = j0.01$

then

$$[Y] = \begin{bmatrix} -j10 & 0 & j10 & 0 \\ 0 & -j10 & 0 & j10 \\ j10 & 0 & -j19.99 & j10 \\ 0 & j10 & j10 & -j19.99 \end{bmatrix}$$

$\swarrow A_{11}$ $\swarrow A_{12}$
 $\nwarrow A_{21}$ $\nwarrow A_{22}$

$$[Y'] = [A_{11}] - [A_{12}][A_{22}]^{-1}[A_{21}]$$

$$= -j10 \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - j10 \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} -j19.99 & j10 \\ j10 & -j19.99 \end{bmatrix}^{-1} (j10) \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

2x2 Identity Matrix


$$= -j10 [I] - (j10) [I] \begin{bmatrix} -j19.99 & -j10 \\ -j10 & -j19.99 \end{bmatrix} (j10) [I]$$

-299.6

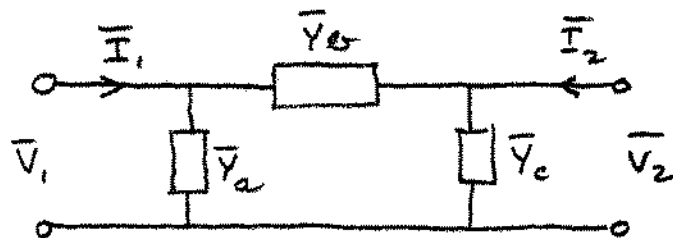(36)

$$[Y'] = \begin{bmatrix} -j3.328 & j3.338 \\ j3.338 & -j3.328 \end{bmatrix}$$

Let the following π network be used to realize the admittance matrix $[Y']$



Solve for \bar{Y}_a , \bar{Y}_b & \bar{Y}_c in the diagram above

$$\left. \begin{aligned} \bar{I}_1 &= \bar{Y}_a \bar{V}_1 + \bar{Y}_b (\bar{V}_1 - \bar{V}_2) \\ \bar{I}_2 &= \bar{Y}_c \bar{V}_2 + \bar{Y}_b (\bar{V}_2 - \bar{V}_1) \end{aligned} \right\} \Rightarrow \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix} = \begin{bmatrix} \bar{Y}_a + \bar{Y}_b & -\bar{Y}_b \\ -\bar{Y}_b & \bar{Y}_b + \bar{Y}_c \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix}$$

$$\therefore \bar{Y}_b = -j3.338 \Rightarrow \bar{Z}_b = j0.2996 \text{ (inductive)}$$

$$\bar{Y}_a + \bar{Y}_b = -j3.328 \Rightarrow \bar{Y}_a = j0.01 = \bar{Y}_c \text{ (capacitive)}$$

